


# EECS 251A: Team 6

*Eric Wu & Lisa Qing*

# Implementation

*CPU & Cache & Baseline Results*

# 3-Stage Pipeline Diagram

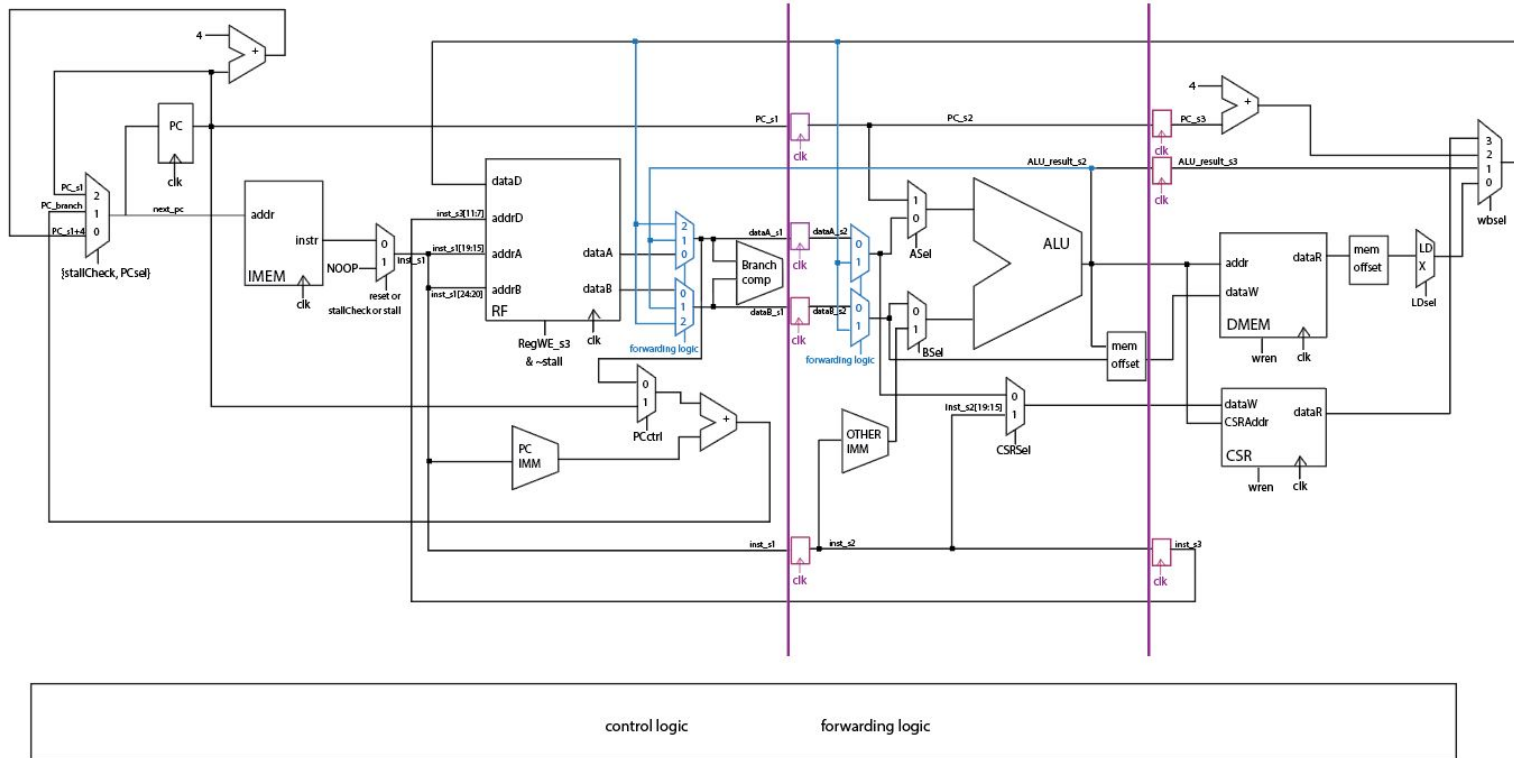


# 3-Stage Pipeline Diagram

## *Design Choices*

1. Stages: IF & D | EX | MEM & WB
2. Branch comparator at Decode stage
  - a. Pro: less control hazards
  - b. Con: longer critical path, extra forwarding muxes for branch comparator, and requires 1 stall for a load then branch/jump instruction

# Post-Synthesis Critical Paths

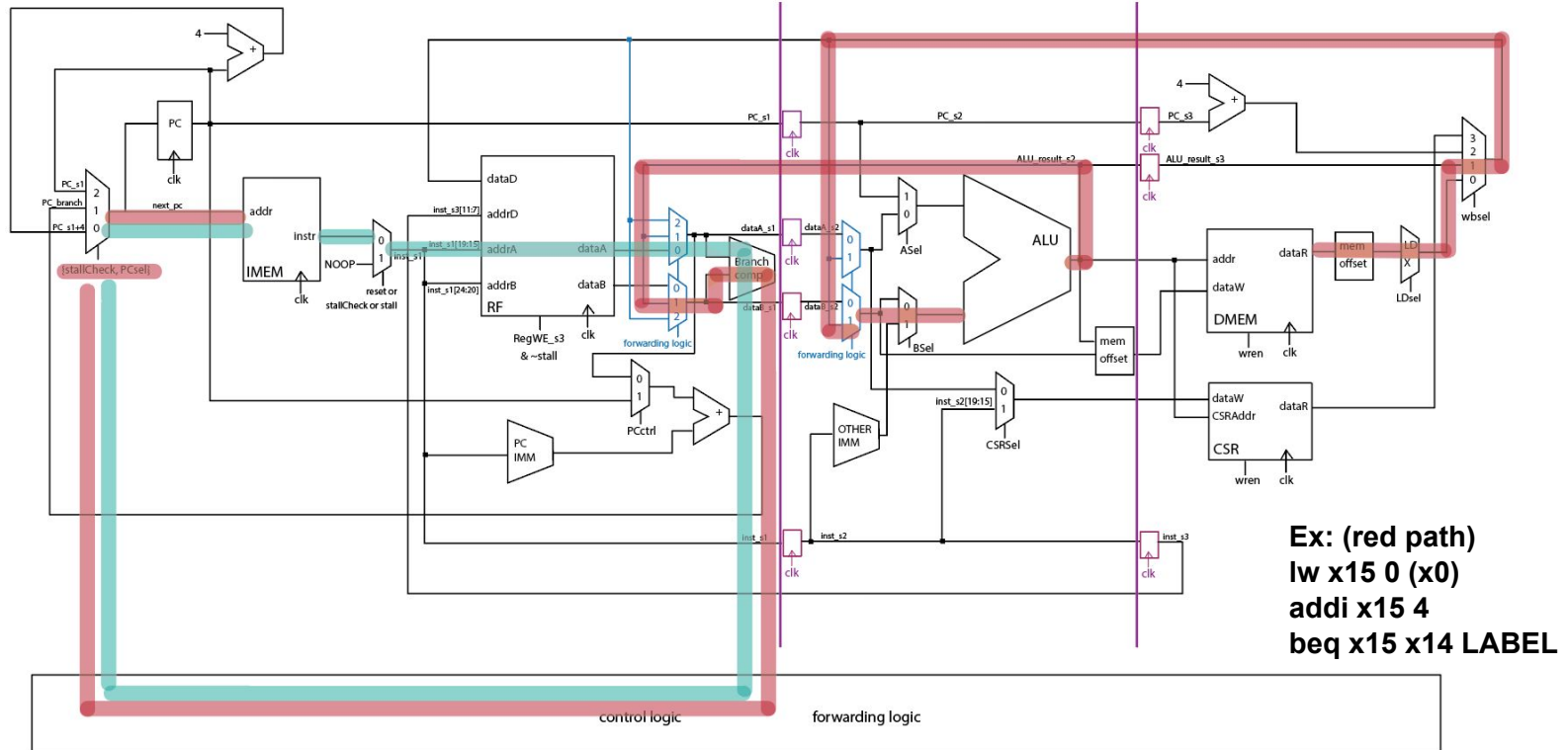


# Cache Block Diagram

Two modules:


- Cache controller (FSM logic)
- Cache array

Additional Note:

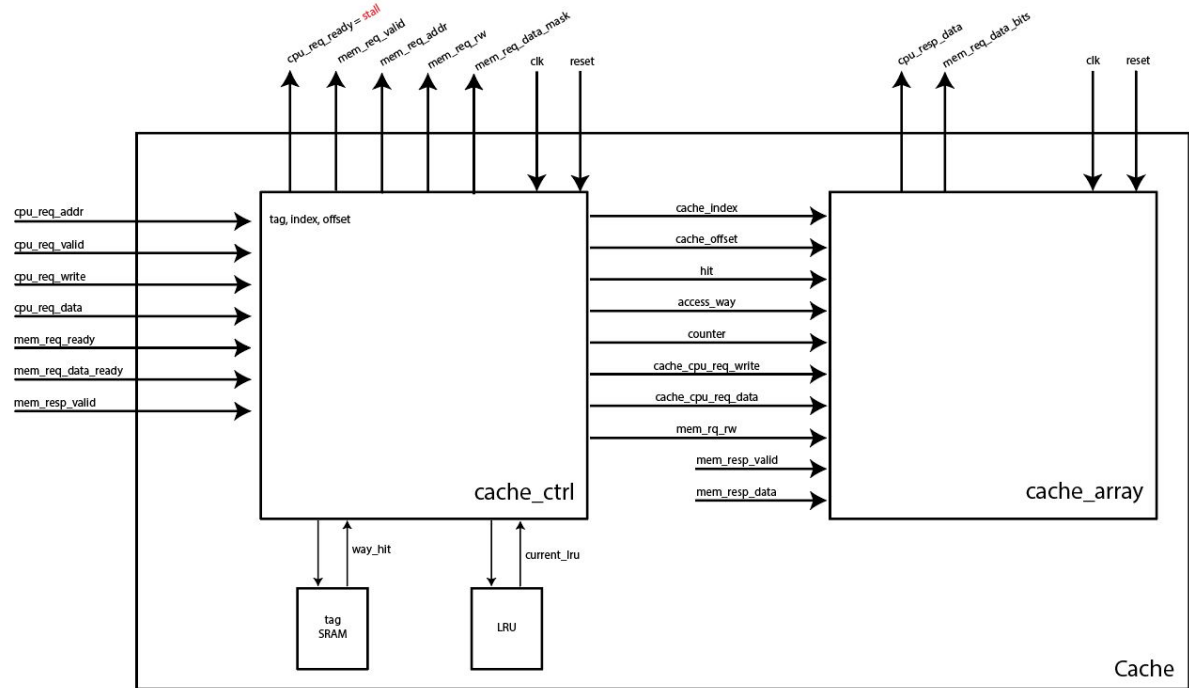- Accessing cache will stall all stages in the CPU
- LRU Replacement Policy



# Cache Design (2-way 1kB example)

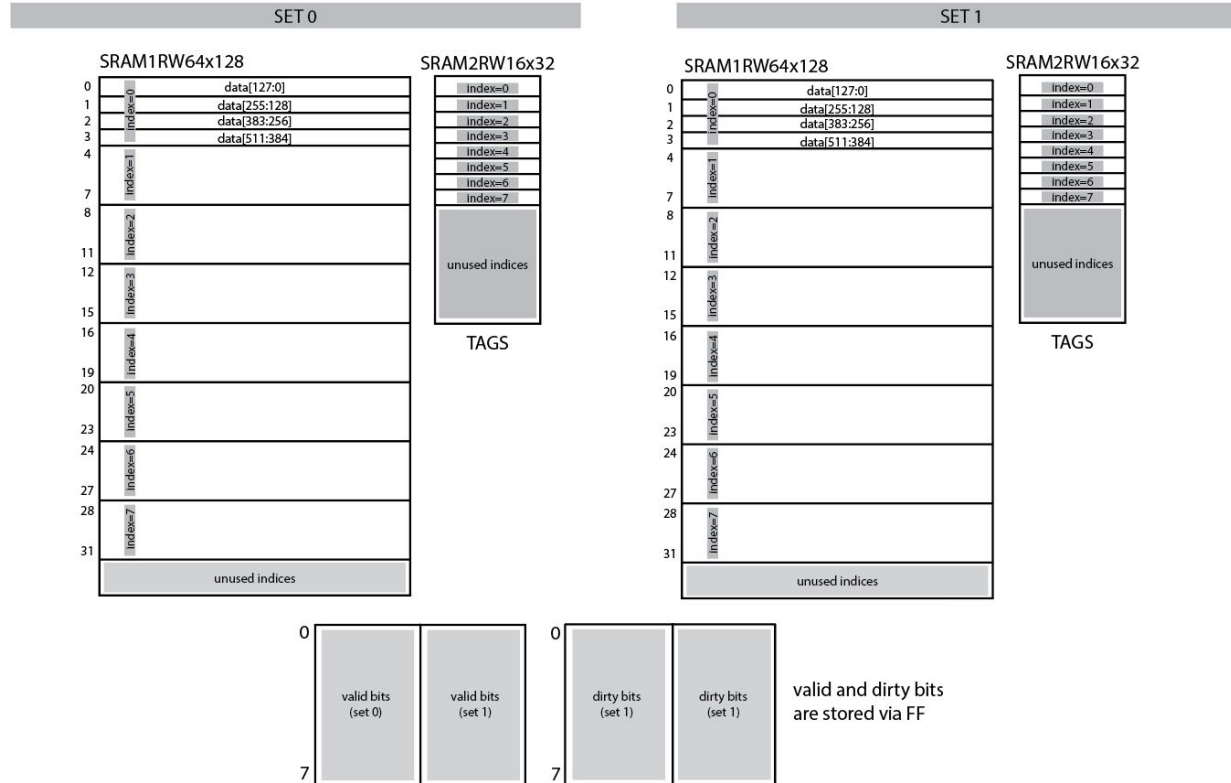


# Cache FSM

Hit Time → 2 cycles

Refill Penalty → 8 cycles

Eviction Penalty → 16 cycles

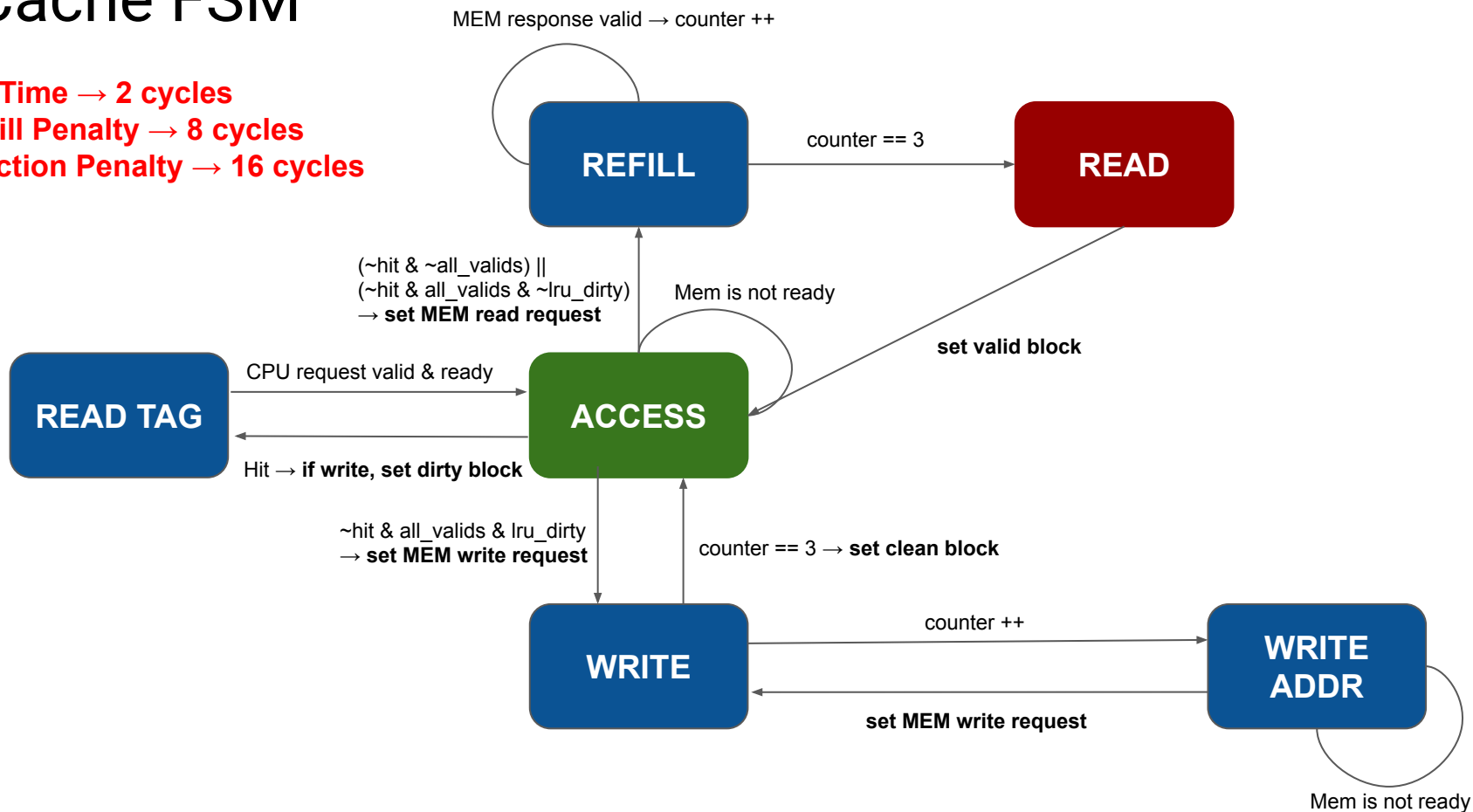



# Baseline Results (RTL-SIM)

1kB Direct-mapped cache with (1RW tag ram & 1RW data ram w/o bytemask)	
cachetest	5,051,096
final	15,325
fib	13,954
sum	31,866,236
replace	31,605,032

```
[ PASSED ] /home/cc/eecs151/fa20/class/eecs151-aar/project_skeleton/bmark_output/cachetest.out      () after 5051096 simulation cycles
[ PASSED ] /home/cc/eecs151/fa20/class/eecs151-aar/project_skeleton/bmark_output/final.out      () after 15325 simulation cycles
[ PASSED ] /home/cc/eecs151/fa20/class/eecs151-aar/project_skeleton/bmark_output/fib.out       () after 13954 simulation cycles
[ PASSED ] /home/cc/eecs151/fa20/class/eecs151-aar/project_skeleton/bmark_output/sum.out      () after 31866236 simulation cycles
[ PASSED ] /home/cc/eecs151/fa20/class/eecs151-aar/project_skeleton/bmark_output/replace.out  () after 31605032 simulation cycles
```

# Floorplan (1kB DM) $\rightarrow 470 \times 550 \mu\text{m}^2$

- Design density (pre-filler) : 13.9%



# Timing Report (1kB DM)

- Min cycle time: 0.97ns



```
Path 1: MET (1.113 ps) Setup Check with Pin mem/dcache/c_ctrl/tag_dirty_reg[4][0]/CLK->D
View: PVT_0P63V_100C.setup_view
Group: reg2reg
Startpoint: (R) mem/icache/c_array/array_offset_reg[0]/CLK
Clock: (R) clk
Endpoint: (R) mem/dcache/c_ctrl/tag_dirty_reg[4][0]/D
Clock: (R) clk

      Capture      Launch
Clock Edge:+ 970.000      0.000
Src Latency:+ -142.690    -142.690
Net Latency:+ 144.100 (P) 156.200 (P)
Arrival:= 971.410      13.510

      Setup:-      3.687
Uncertainty:- 100.000
Copr Adjust:+ 0.000
Required Time:= 867.723
Launch Clock:= 13.510
Data Path:+ 853.100
Slack:= 1.113
Timing Path:
```

# Floorplan (1kB 2-way) $\rightarrow 490 \times 800 \mu\text{m}^2$

- Design density (pre-filler) : 6%

  



# Timing Report (1kB 2-way)

- Min cycle time: 1.07 ns

```
Path 1: MET (1.146 ps) Setup Check with Pin mem/dcache/c_ctrl/tag_dirty_reg[2][0]/CLK->D
View: PVT_0P63V_100C.setup_view
Group: reg2reg
Startpoint: (R) mem/dcache/c_array/array_set_reg[0]/CLK
Clock: (R) clk
Endpoint: (R) mem/dcache/c_ctrl/tag_dirty_reg[2][0]/D
Clock: (R) clk

          Capture      Launch
Clock Edge:+ 1070.000      0.000
Src Latency:+ -164.507    -164.507
Net Latency:+ 177.300 (P) 189.600 (P)
Arrival:= 1082.793      25.093

Setup:- 6.055
Uncertainty:- 100.000
Copr Adjust:+ 0.000
Required Time:= 976.738
Launch Clock:= 25.093
Data Path:+ 950.500
Slack:= 1.146
Timing Path:
```

# Optimization

*Cycle Counts & Critical Path*

# Optimization

## Optimizing for number of cycles

1. Using 2RW tag ram instead of 1RW tag ram → less access cycles
2. Byte mask data ram → less penalty in cache miss by removing READ state
3. Different Cache Configuration → less miss rate

## Optimizing for frequency (Critical path: lw → add → beq with data forwarding)

1. Change SRAM macros positions in the floorplan
2. Set false path from mem\_req\_ready (large delay) → muxwb
3. Move branch comparator to EXE stage and add branch predictor

# Cache Configuration Comparison (RTL-SIM)


Chart illustrates the % speed up (cycle count optimization) for different cache sizes & set associativity for **2RW Tag Ram w/ Byte Mask Data Ram**

Baseline (1kB DM Cache w/ 1RW Tag Ram w/o Byte Mask): **31,866,236**

Best Result (4kB 4-way Cache w/ 2RW Tag Ram w/ Byte Mask): **27,371,328**

**14.1 % speed up**

Cache Comparison Chart (sum.out)

 



# Final Results (cycle counts \* min cycle time)

Execution time = Cycle counts \* min cycle time

Cache Configuration (baseline): 1kB DM w/ **1RW tag ram w/o mask**

- Exec. Time =  $31,866,236 * 0.97 = \mathbf{30.910\ ms}$

Cache Configuration (optimized): 1kB 2-way w/ **2RW tag ram w/o mask**

- Exec. Time =  $27,713,413 * 1.07 = \mathbf{29.653\ ms}$
- Optimized cycle count trade off with frequency
  - Larger memory may require longer access time

**Overall 4.07% speed up**

# Obstacles

*Bugs & How we resolve them*

# Major Bugs

- Load to branch data hazard
  - Insert noop if these instructions are found and stall PC
    - However, this instruction stall that inserts noops is different from the memory stall, which needs to keep the current instructions in the pipeline
- Reading garbage initial data of valid and dirty bits from SRAM
  - SRAM doesn't have a "reset" → use flip-flops instead (separate from tag SRAM)
- CPU write miss to cache
  - At most we only write 32 bits to cache, but each entry in the SRAM is 128 bits
    - Must refill then read to get the present data then mask and write to SRAM
    - Add a READ state after REFILL state
- Area issue
  - Initial design used 16 SRAM2RW16x32 per way → takes a lot of area (38 SRAMS for 2-way)
  - New design to use SRAM1RW64x128 per way (8 SRAMS for 2-way)

# Debug Schemes

1. Monitor the signals via testbench (log file)
2. Verify the content in the register files to see which parts of the assembly fails
3. Breakdown the C program into the minimum loop cycles to find the errors
4. Dve to get the current content of the register file and cache

# Q&A

*Thank you!*